

BANGLADESH UNIVERSITY OF BUSINESS AND TECHNOLOGY (BUBT)

Department of Computer Science and Engineering



Rupnagar, Mirpur-2, Dhaka-1216, Bangladesh
Phone: PABX-9024266, 9024277, 9015397, 9020132-4, Fax: 9024399
E-mail: info@bubt.edu.bd, Website: www.bubt.edu.bd

EXAMINATION SCRIPT

(To be filled up by class teacher)

Question No.	Mark Obtained
1	
2	
3	
4	
5	
Total Marks	


(This part is to be filled up by students)

Name:	MD.Sajed
Student ID:	20211103037
Intake & Section:	46 th (01)
Program:	B.Sc. in CSE
Course code:	EEE 101
Course title:	Electrical Technology
Trimester:	Spring 2021
Exam type:	Final Term (Open Book Exam)
Date:	August 03, 2021
Cell No.:	01710073692
Email Address:	Mdsajed001@gmail.com


COs	Q. No.	Total Marks	Marks obtained
CO1	1	5	
CO2	3, 4	20	
CO3	2, 5	15	

Signature of Examiner and Date:


Sub:

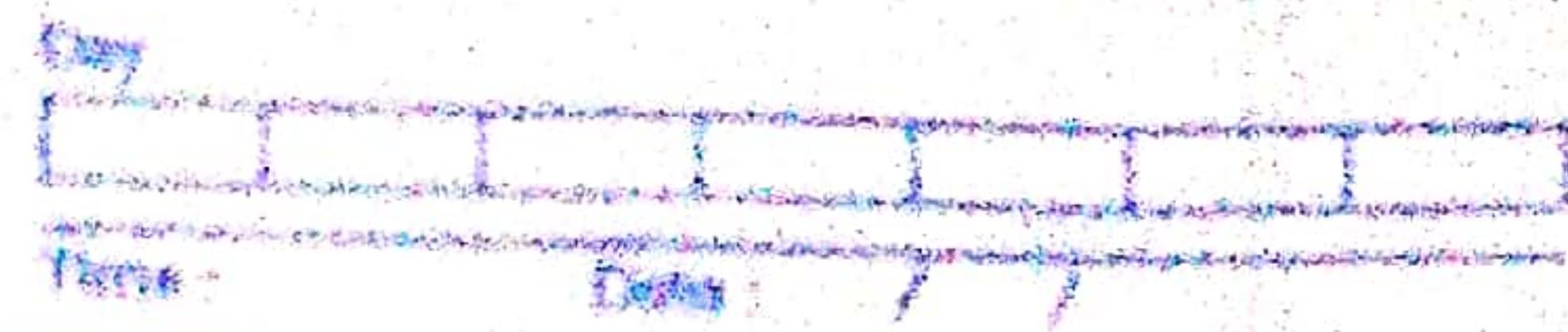


Ans: To the Qs. No. 01(a)

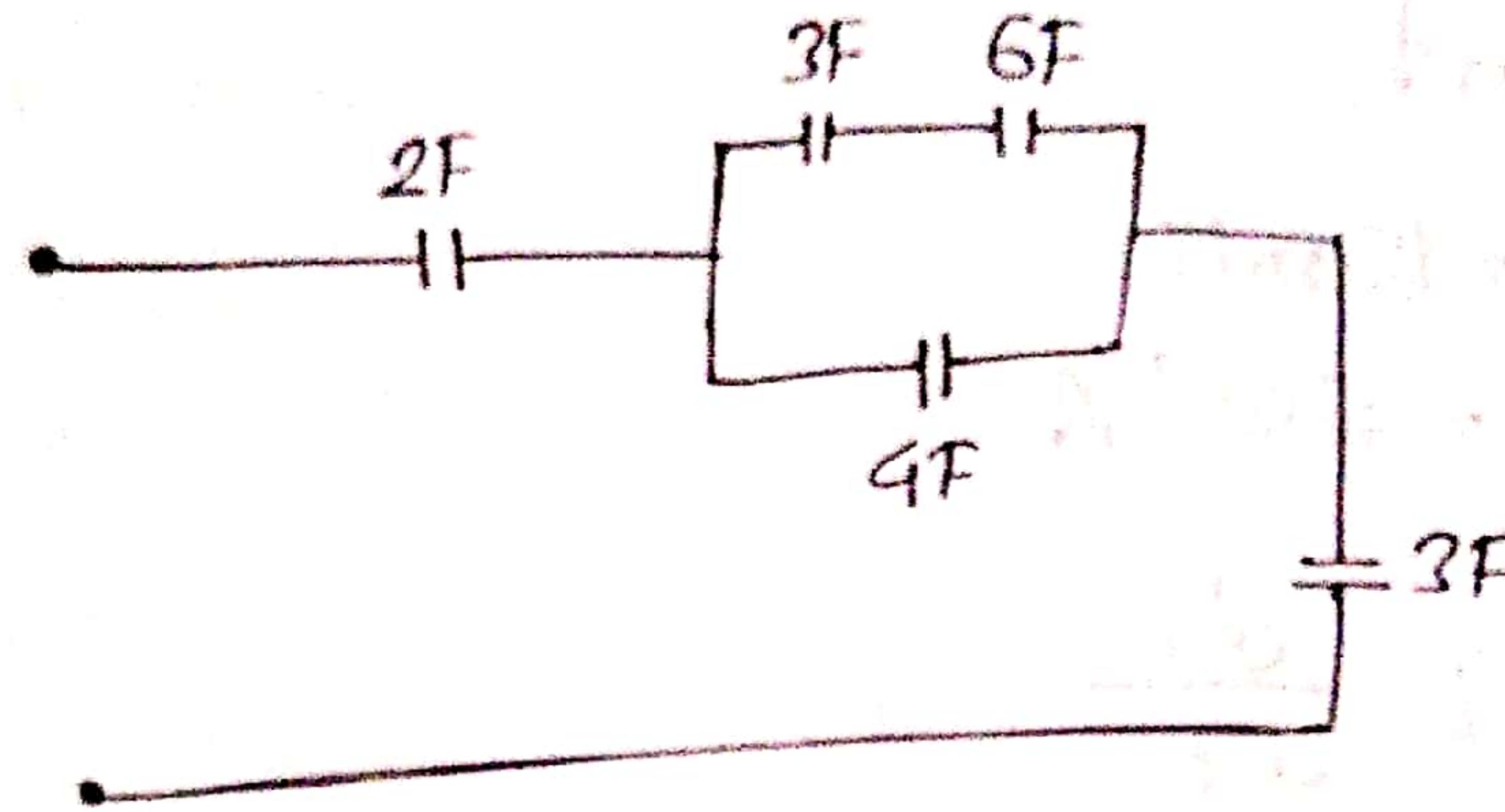
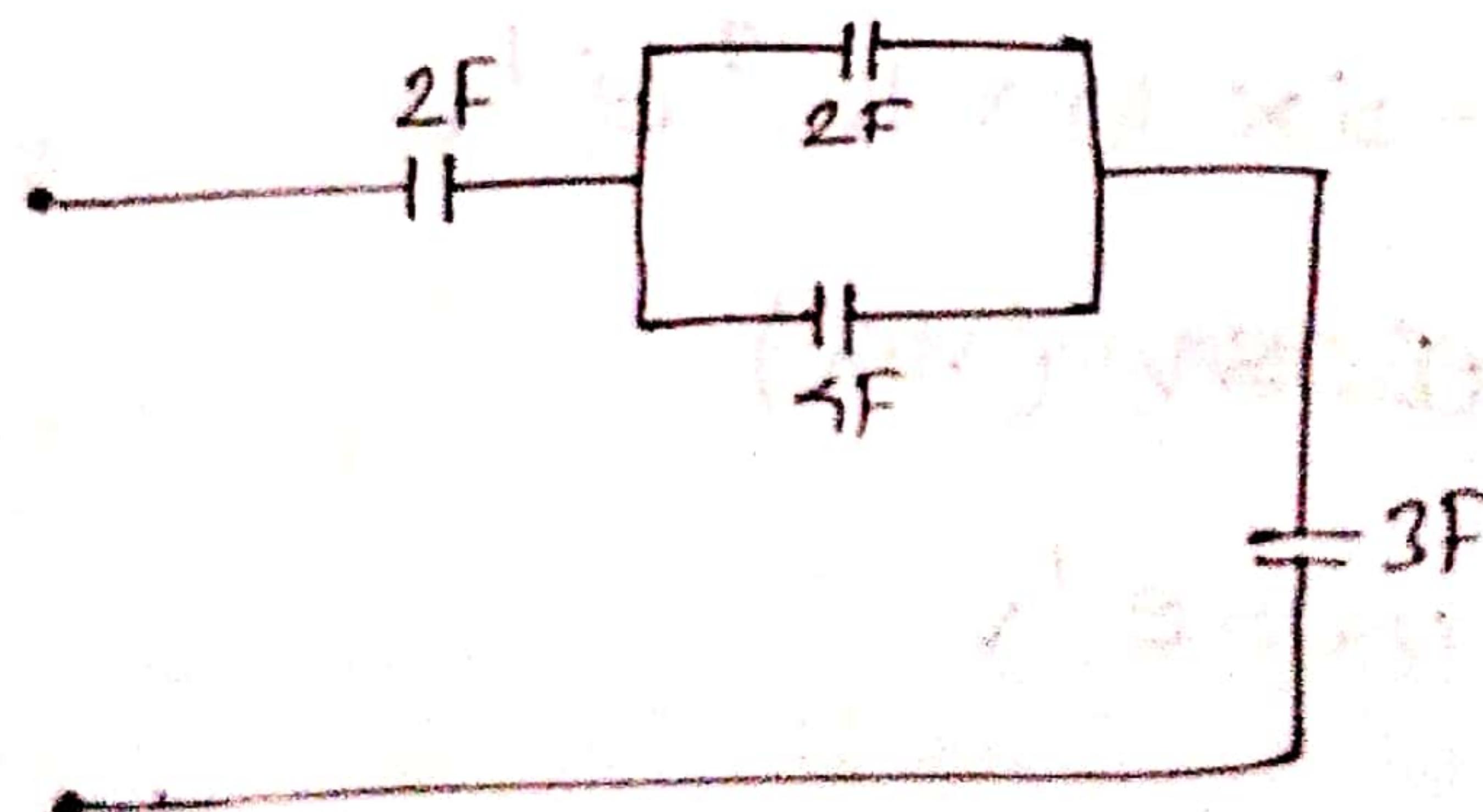
$$\therefore (3^{-1} + C^{-1})^{-1} = 2F$$



$$(2+5)F = 6F$$

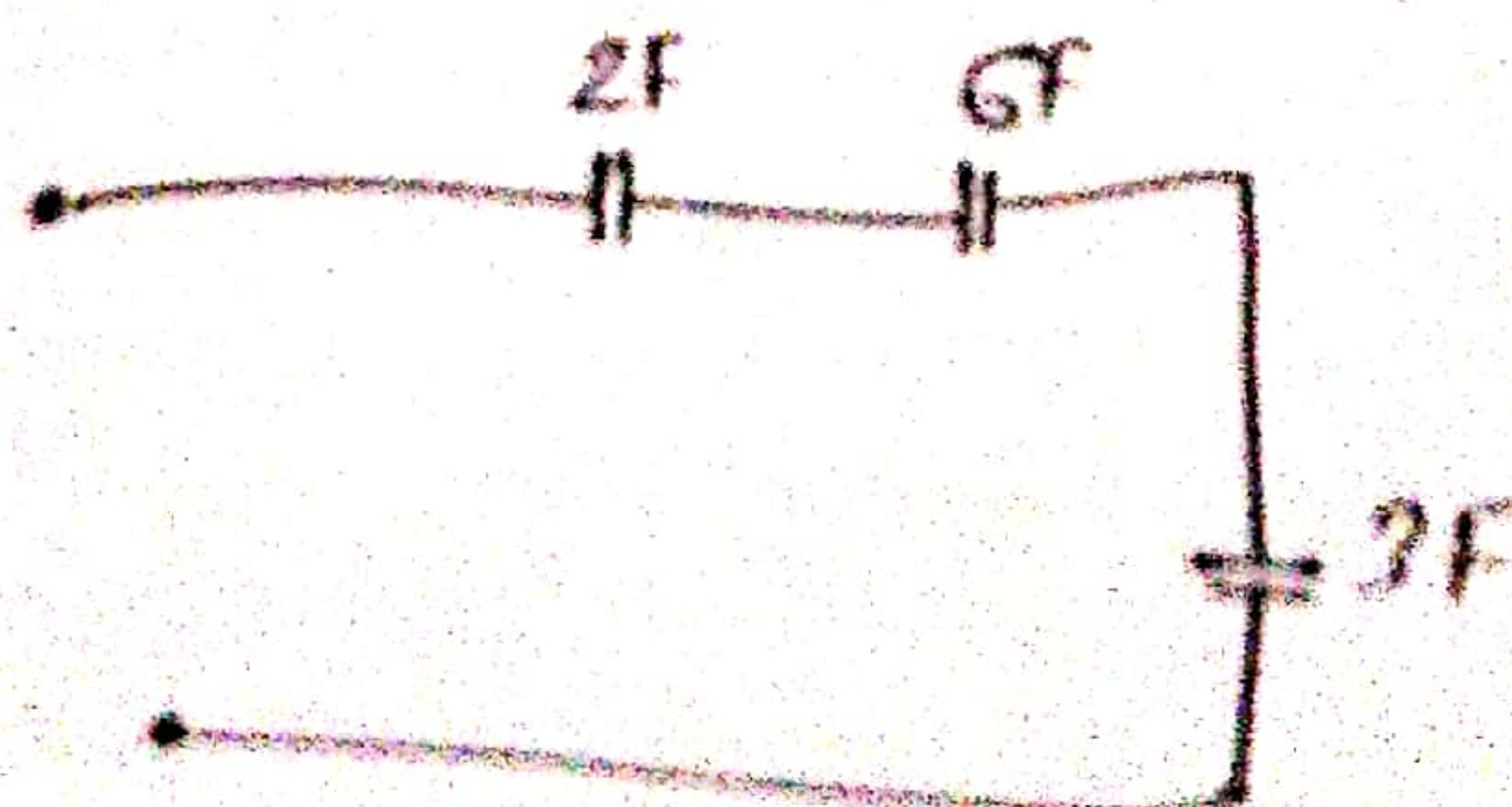

$$\therefore \text{Equivalent capacitor} = (2^{-1} + 6^{-1} + 3^{-1})^{-1} = 1F$$

(Q) Ans No: 01 (b)


Given that,

$$L = 10 \text{ mH}$$

$$I = 5e^{-t} \text{ A}$$

$$\begin{aligned}
 \therefore V(t) &= L \frac{di}{dt} \\
 &= 10 \times 10^{-3} \frac{d}{dt} (5e^{-t}) \\
 &= -5 \times 10 \times 10^{-3} e^{-t} V \\
 &= -0.05 e^{-t} \text{ V} \\
 &= 0.05 e^{-t} \text{ V}
 \end{aligned}$$

Ans to the Qs. No 1(c)

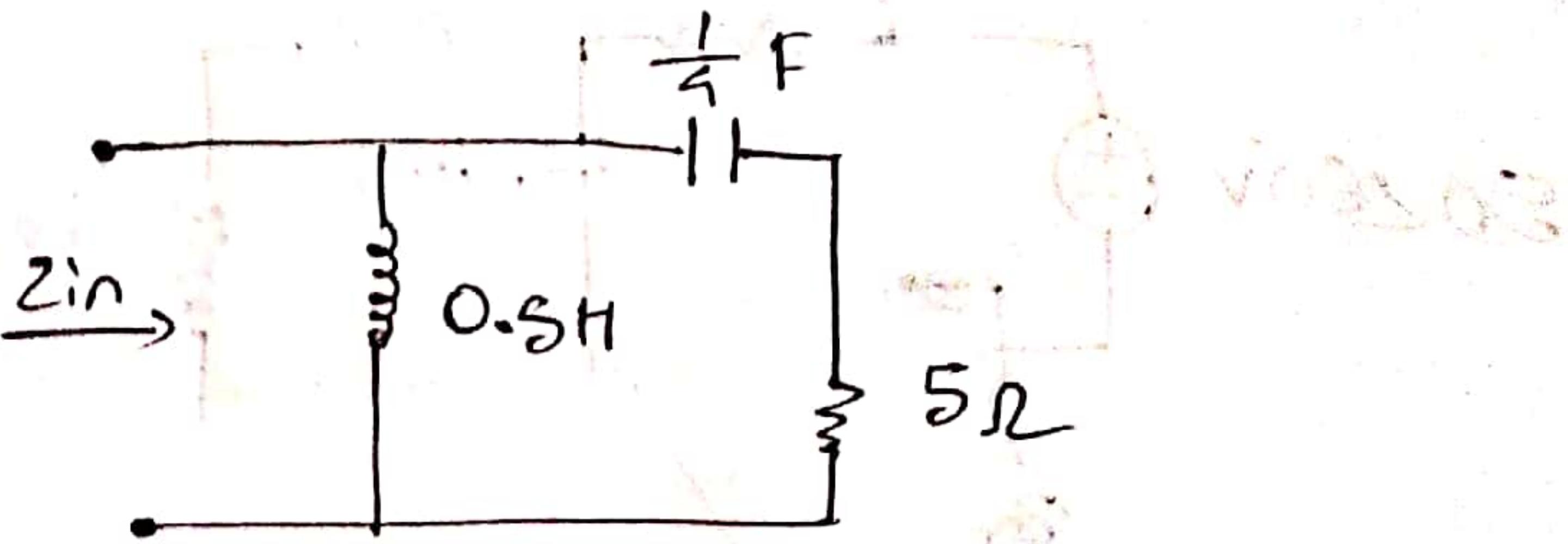

Given that,

$$\omega = 3 \text{ rad/s}$$

$$\text{Here, } \omega_L = j\omega L \\ = j \times 3 \times 0.8 = j2.55 \Omega$$


$$X_C = \frac{1}{j\omega C}$$

$$= \frac{1}{j \times 3 \times \frac{1}{4}} = -j0.8 \Omega$$

$$Z_{in} = (C(j2.5) + (-j0.8 + s))^{-1}$$

$$= (1.12 + j2.12) \Omega$$
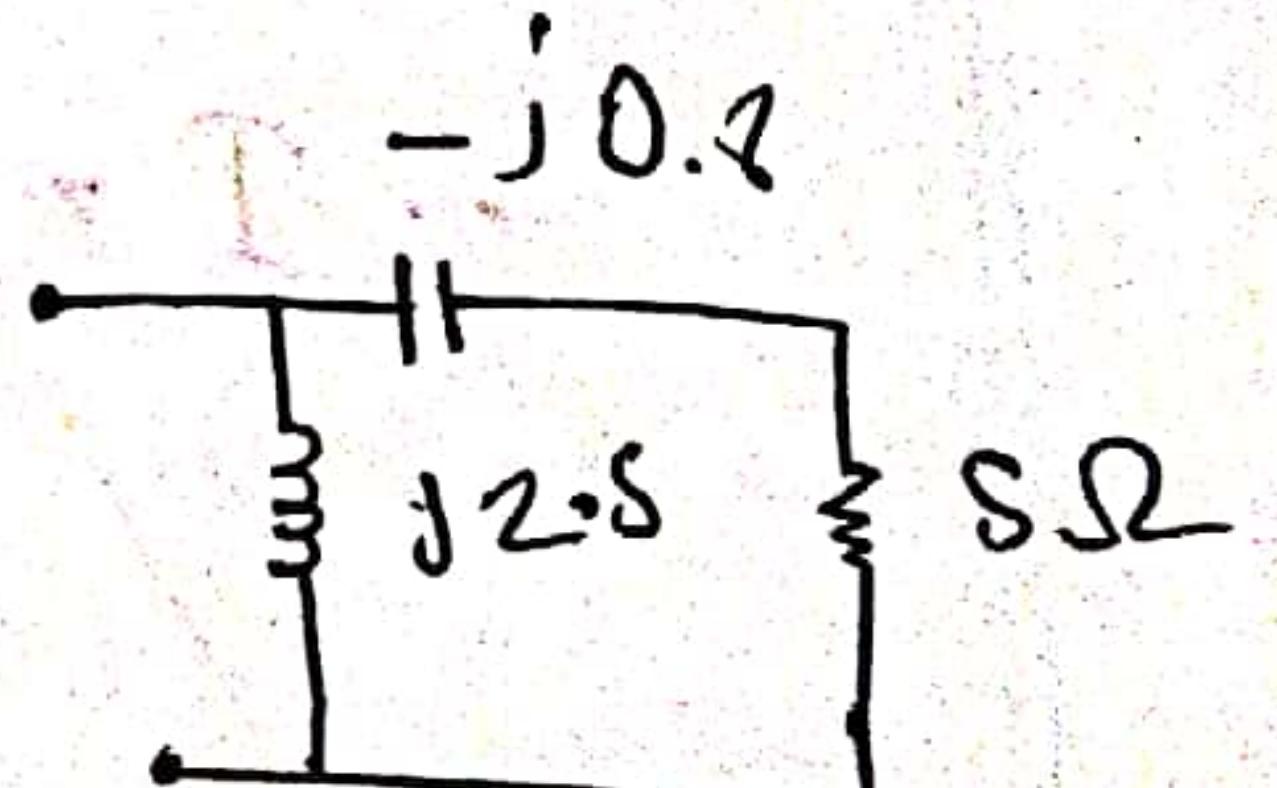
$$= 2.5 \angle 62.13^\circ \text{ (Ans)}$$



Ans to the Qs. No. 01(d)

Given that,

$$V_1 = -10 \sin(\omega t - 10^\circ) V$$

$$V_2 = 10 \cos(\omega t + 10^\circ) V$$

we knew,

$$V_A = V_m \cos(\omega t + \phi)$$

$$V_{1,2} = 10 \sin(\omega t - 10^\circ) V$$

$$= 10 \cos(\omega t - 10^\circ + 90^\circ) v$$

$$= 10 \cos(\omega t + 180^\circ) v$$

$$V_2 = 10 \cos(C\omega t + 10^\circ) V$$

phase difference $\approx Q_1 - Q_2$

$$= (180^\circ - 10^\circ)$$

$$= 170^\circ$$

16

V₁ Leads V₂ by 120° (Ans)


Sub:

Date

Time:

Date:

Ans to the Qs No 01 (e)

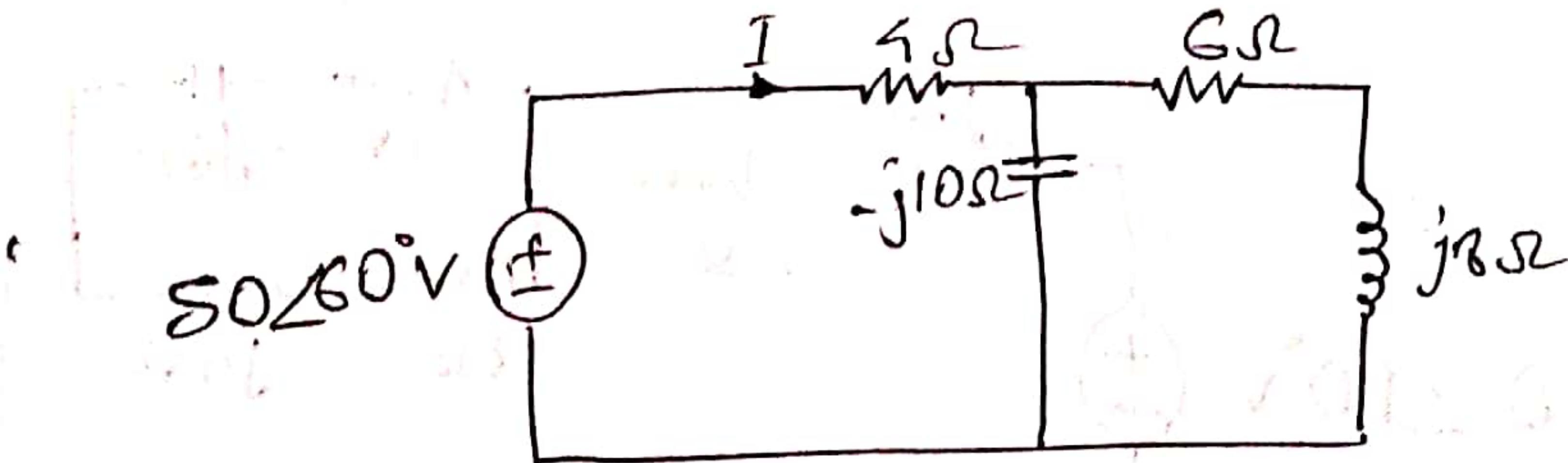

Here,

$$\omega = 0 \text{ rad/s}$$

$$\therefore Z_1 = 1 + (1-j10)^{-1} + (6+j8)^{-1} \parallel^{-1}$$

$$= 10 - j5$$

$$= 10.65 \angle -19.79^\circ$$

$$\therefore I = \frac{V}{Z} = \frac{50\angle 60^\circ}{10.65 \angle -19.79^\circ}$$

$$= 2.54 \angle 74.75^\circ$$

$$(2.54 \angle 74.75^\circ) \times (1 + j8)$$

$$= (2.54 \angle 74.75^\circ) \times (1 + j8)$$

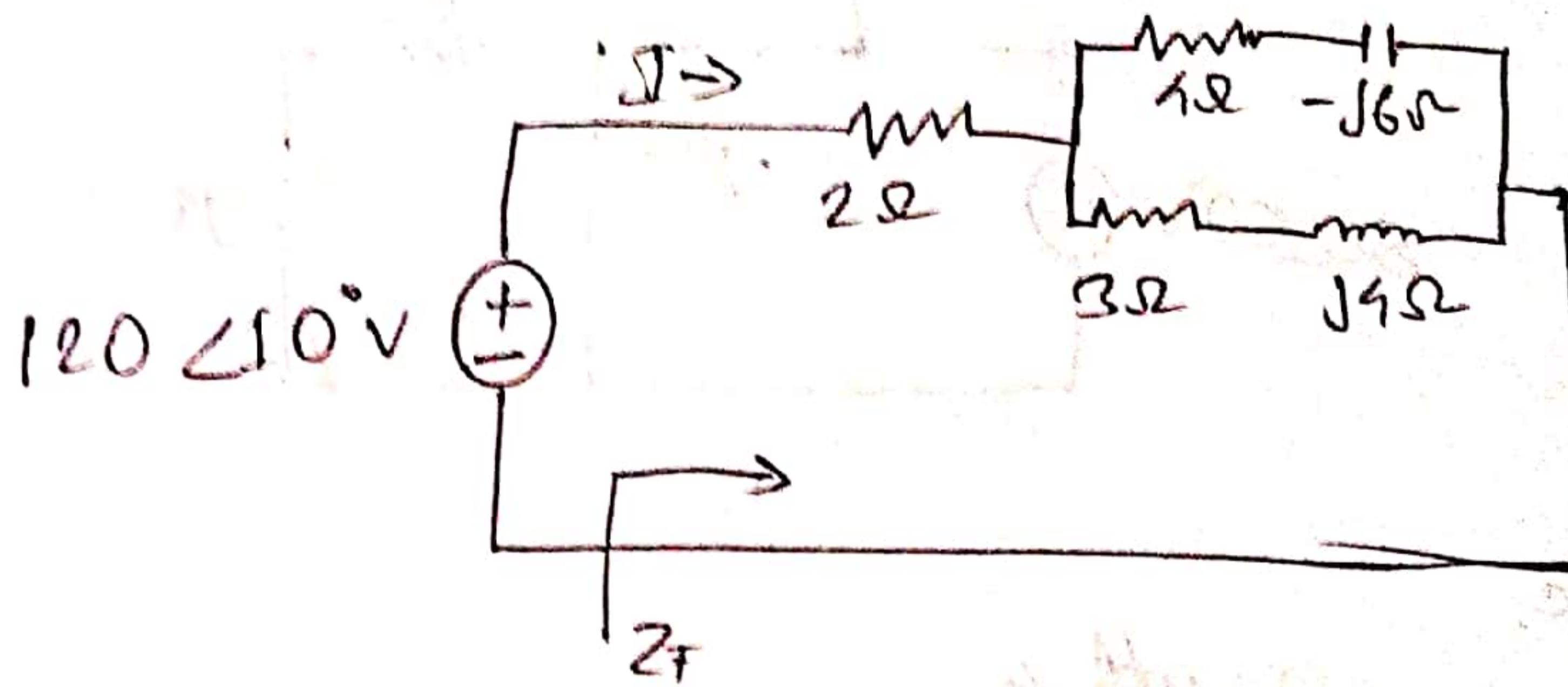
Anode Q.N.2(a)


Fig = 1

From the Figure 1 the total impedance is

$$\begin{aligned}
 Z_I &= 2 + (4+j6) || (3+j4) \\
 &= 2 + \frac{(4-j6)(3+j4)}{(4-j6)+(3+j4)} \\
 &= 2 + \frac{(4+3+j5)-5(j3+j4)}{(4-j6)+(3+j4)} \\
 &= 2 + \frac{(12+j16-j18+2j)}{7-j2} \\
 &= 2 + \left(\frac{36-j2}{7-j2} \right) \\
 &= 6.83 + j1.00 \Omega
 \end{aligned}$$

Sub:

Copy

Print

Scan

The total impedance in the circuit Z_T is $= 6.83 + j1.09 \Omega$

The current flowing in the circuit is

$$I = \frac{V}{Z_T}$$

$$= \frac{120 \angle 10^\circ}{6.83 + j1.09}$$

$$= 17.34 + j0.27$$

$$= 17.34 \angle 0.9^\circ A$$

Ans


Sub:

Day _____
 Time : _____ Date : / /

Arun Dc Mc Qs M. 06

$$x = (37 + 2) \Omega$$

$$= 39 \Omega$$

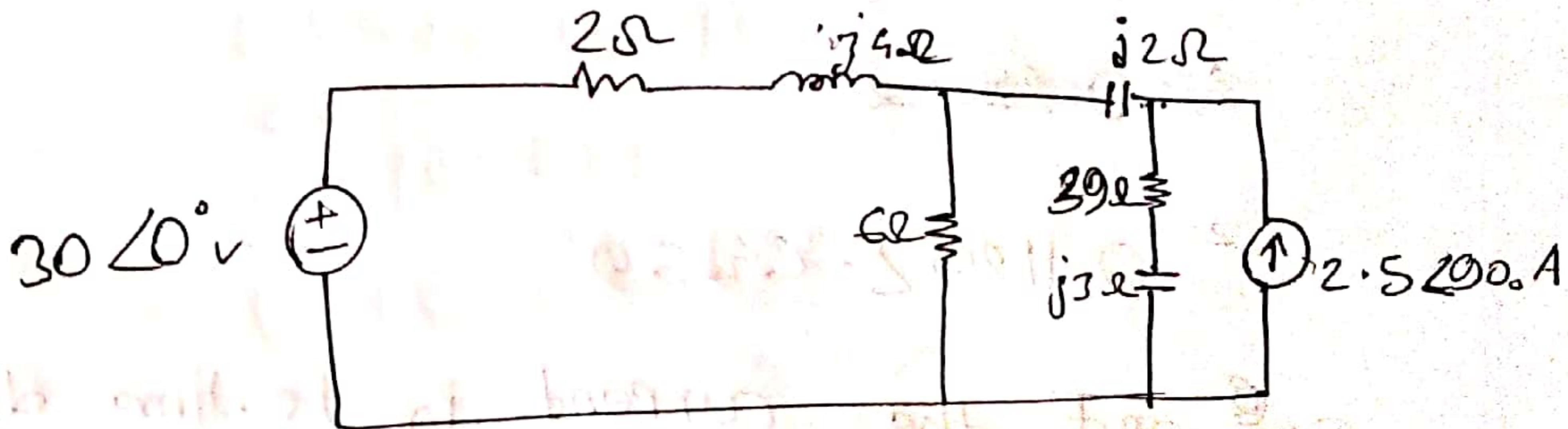

We transform the voltage source to current source

source


$$I_s = \frac{30\angle 0^\circ}{2+j4}$$

$$= 3 - j6 \text{ A}$$

Sub:

Day _____
 Time : _____ Date : _____

Now,

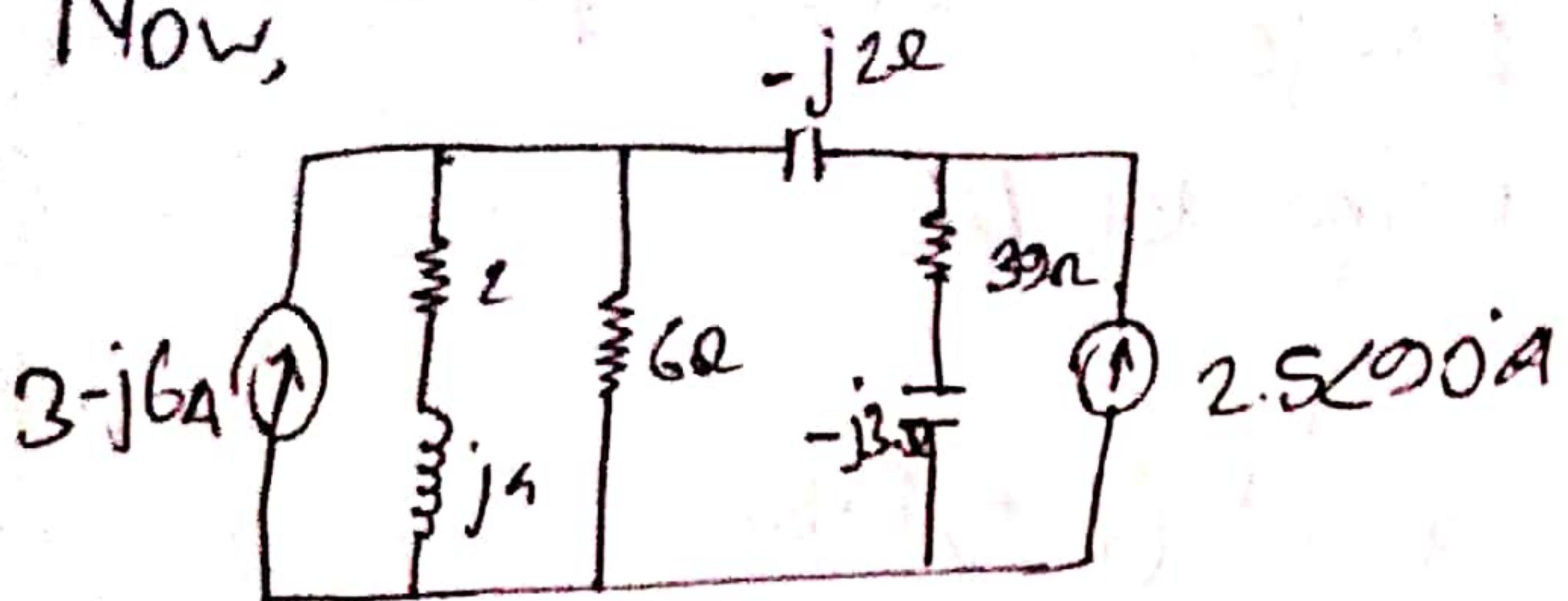

Now,

$$Z_s = G \parallel (2 + j4)$$

$$= \frac{6(2 + j4)}{8 + j4}$$

$$= \frac{12}{5} + \frac{24}{5}j = 2.4 + j1.8$$


Therefore,

$$\begin{aligned} V_s &= I_s \times Z_s \\ &= (3 - j6) \times (2.4 + j1.8) \\ &= 18 - j0 \end{aligned}$$

$$\text{Here, } 2.5 \angle 90^\circ A = j2.5 A$$

From fig(b).
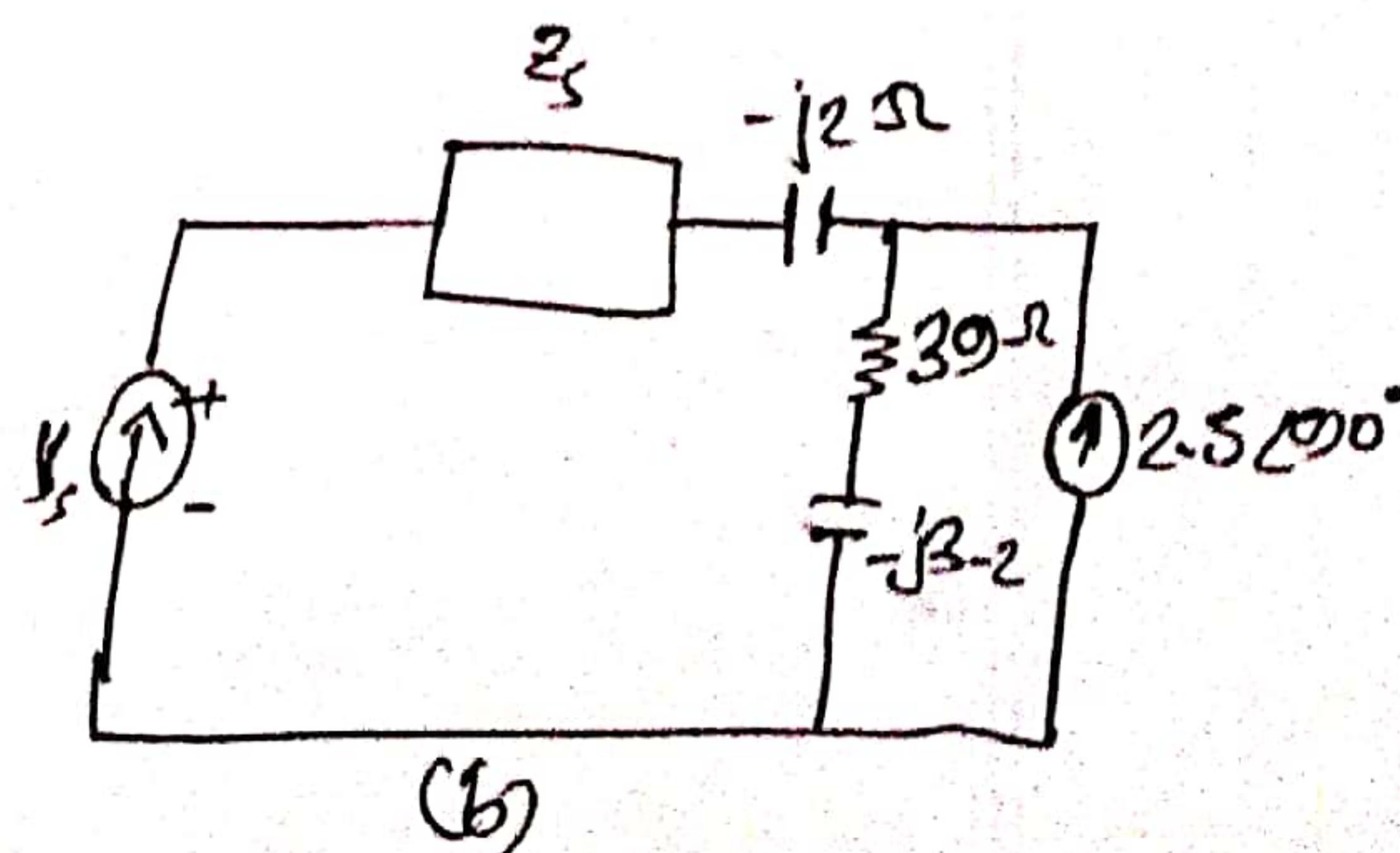
$$\begin{aligned} Z_0 &= 2s - j2 \\ &= 2.4 + j1.8 - j2 \\ &= 2.4 - j0.2 \end{aligned}$$



(b)

Sub:

Day _____
 Time : / / Date : / /

$$\text{So, } I_o = \frac{V_s}{Z_0} = \frac{18 - j0}{2.4 - j0.2} = 7.76 - j3.103 \text{ A}$$


From fig(c) By using CDR,

$$I_u = \left(\frac{Z_0}{Z_0 + 2j - j3} \right) \times (I_o + j2.5)$$

$$= \frac{2.4 - j0.2}{2.4 - j0.2 + 2j} \times (7.76 - j3.103 + j2.5)$$

~~= 6.0106728 +~~

$$= 0.91 < -0.22029^\circ \text{ A}$$

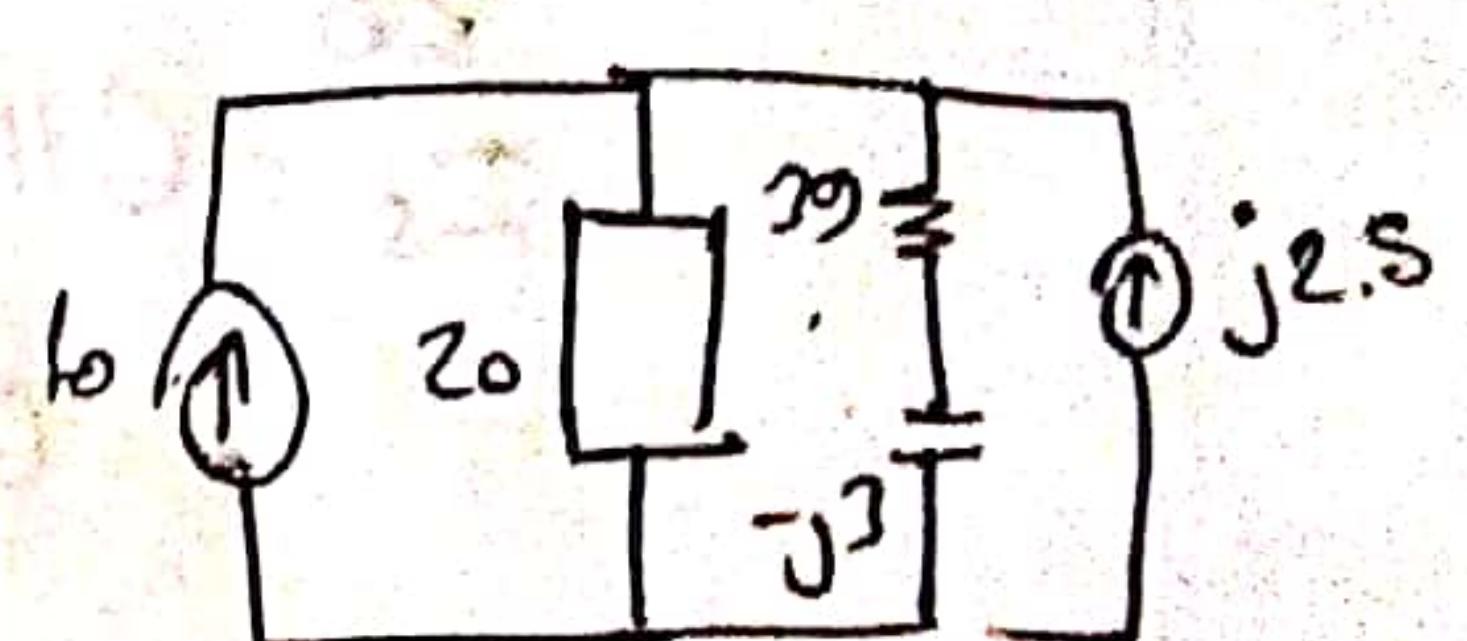

Ans to the Qs. No. 4 (a)

The total current due to acting of both sources is

$$i_o = i_{o1} + i_{o2}$$

i_{o1} is the response due to $8V$ DC source and

i_{o2} is the current due to $6 \cos(4t)V$

Ac source

the bld i_{o1} set ac source value & to zero. In a steady state inductor acts like a short circuit.

$$\text{My id } \approx 37 + j2.38 \Omega$$

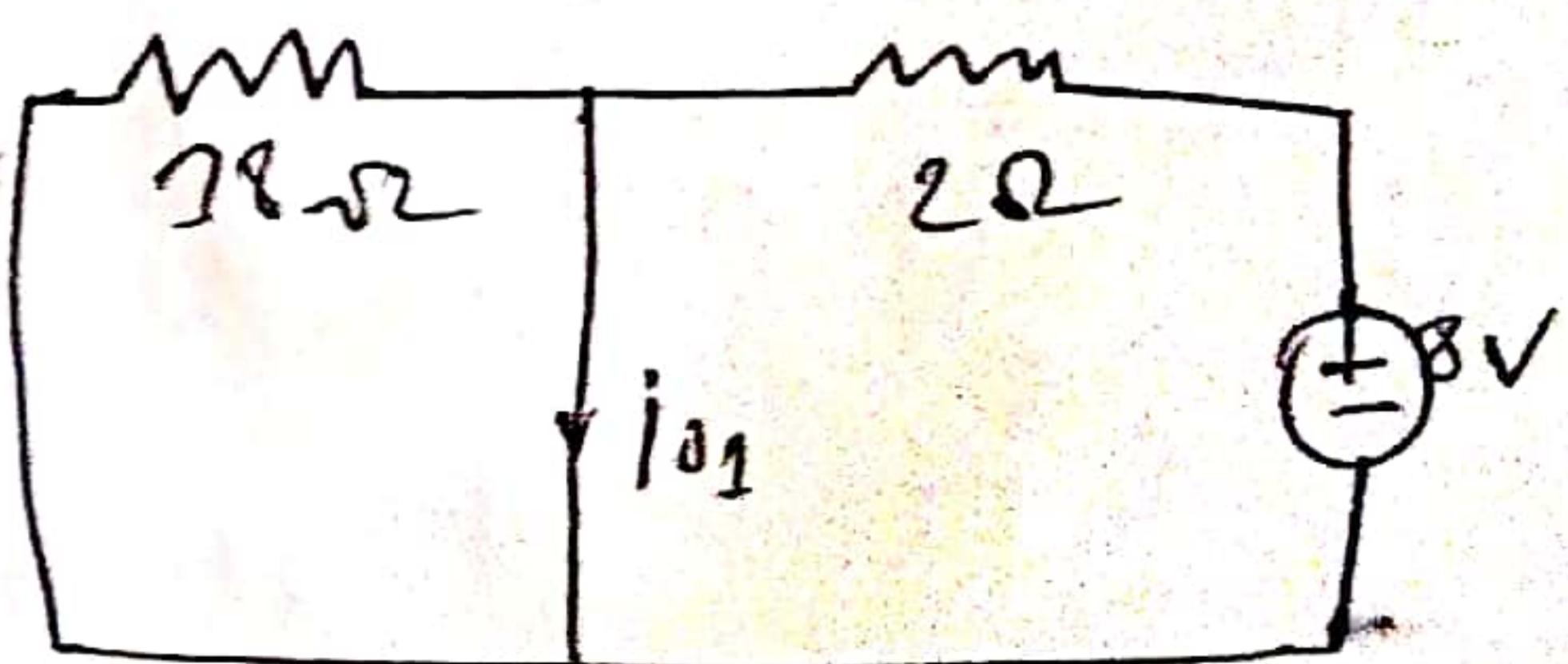


Fig 1

Since 4Ω resistor is connected in parallel with short circuit.

current i_{01}

$$i_{01} = \frac{8}{2}$$

$$= 4A$$

Therefore the current i_{01} due

to $8V$ DC source is $4A$

To find i_{02} , set DC voltage

to zero and transform the circuit into frequency domain.

$$\omega = 4 \text{ rad/s}$$

The posor $i_{02}(j\omega)$

Inductor

$$x_L = j\omega L$$

$$= j(4)(1)$$

$$= j4\Omega$$

shorting method

Sub:

Day					
Time					
Date					

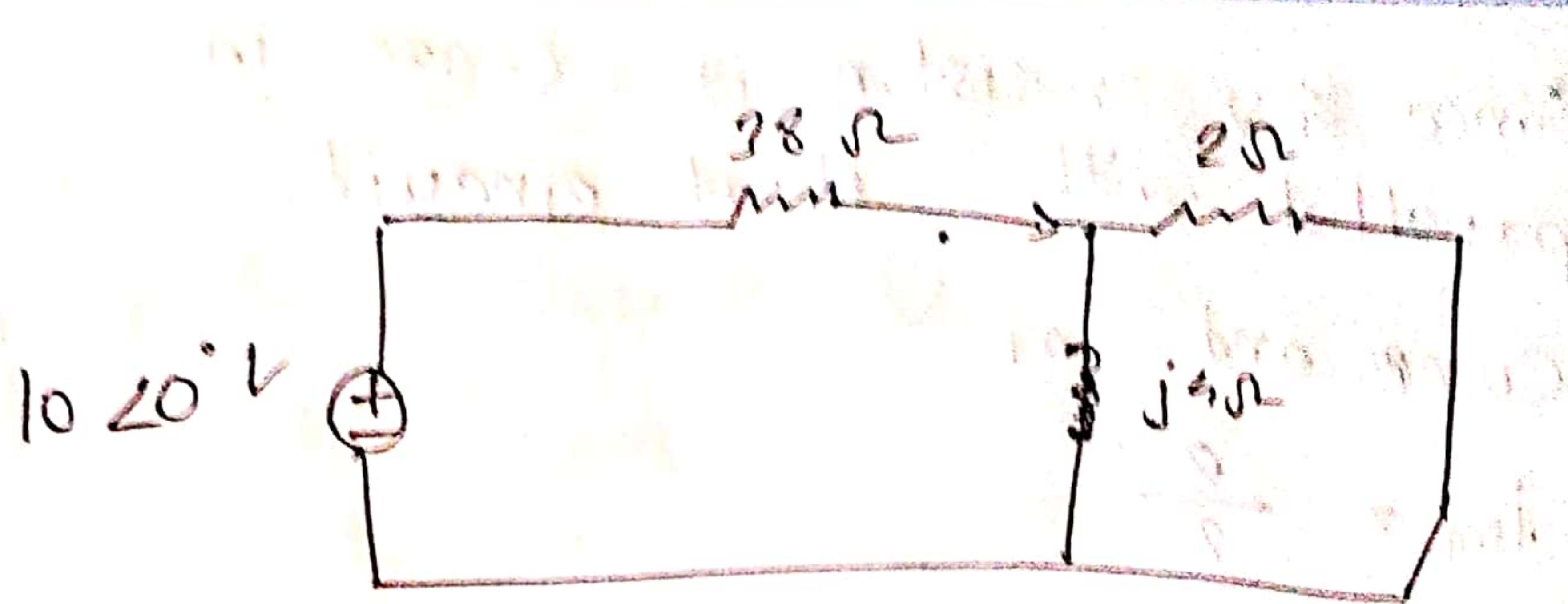


Fig 2e

$$Z_T = 38 + (2 + j4)$$

$$= 38 + \left(\frac{2 \times j4}{2 + j4} \right)$$

$$= 38 + \left(\frac{8}{5} + \frac{8}{5}j \right)$$

$$= 39.6 + 0.8j$$

$$I_T = \frac{10 \angle 20^\circ}{Z_T}$$

$$= \frac{10 \angle 20^\circ}{39.6 + 0.8j}$$

$$= \frac{405}{1961} - \frac{10}{1961}j$$

- Calculate the value of current I_{T1} using current division principle

Sub:

Day

--	--	--	--	--	--	--	--	--

Time :

Date : / /

$$i_{02} = \left(\frac{2}{2+j1} \right) I_T$$

$$= \left(\frac{2}{2+j1} \right) \left(\frac{400}{1061} - \frac{10}{1061} j \right)$$

$$= \frac{0.5}{1061} - \frac{0.200}{1061} j$$

~~1.5000591~~

$$= 0.1129 \angle -64.59^\circ$$

Convert the current i_02 to time domain

~~by multiplying with jω~~

$$i_02 = 0.1129 \cos(4t - 64.59^\circ) A$$

total current

$$i_t = i_{12} + i_{02}$$

$$= 4 + 0.1129 \cos(4t - 64.59^\circ) A$$

$$(4t = 0.1129 + 64.59) A$$

The value of current i_0 is $\int 4 + \cos(4t - 64.59) A$

$$4 + 0.1129 \cos(4t - 64.59) A$$

The value of current

$$I_0 \text{ is } [4 + 0.1129 \cos(4t - 64.59) A]$$

Ans to the Qs No. 8

(i) Given that,

$v = x = 037$

$$N = 600$$

$$N_2 = 20$$

i Primacy loud full impact

$$T_1 \approx \frac{25 \times 10^3}{0.37}$$

2 675-675 wpc

~~GD~~

we know that

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$

Hence

$$I_2 \cdot 2 - \frac{N_1}{N_2} \times I_1$$

$$\Rightarrow I_2 = \frac{100}{20} \times \cancel{675.67} \\ = 20270.1 \text{ A}$$

Sub:

Topic

Term 1

Date:

(III) Given that,

$$E_1 = 0.37 \text{ V}$$

$$N_s = 20$$

$$N_p = 600$$

Here


secondary emf $\frac{E_1}{E_2} = \frac{N_p}{N_s}$

$$\Rightarrow E_2 = \frac{E_1 \times N_s}{N_p}$$

$$\Rightarrow E_2 = \frac{0.37 \times 20}{600}$$

$$\Rightarrow E_2 = 1.233 \text{ V}$$

(Ans)

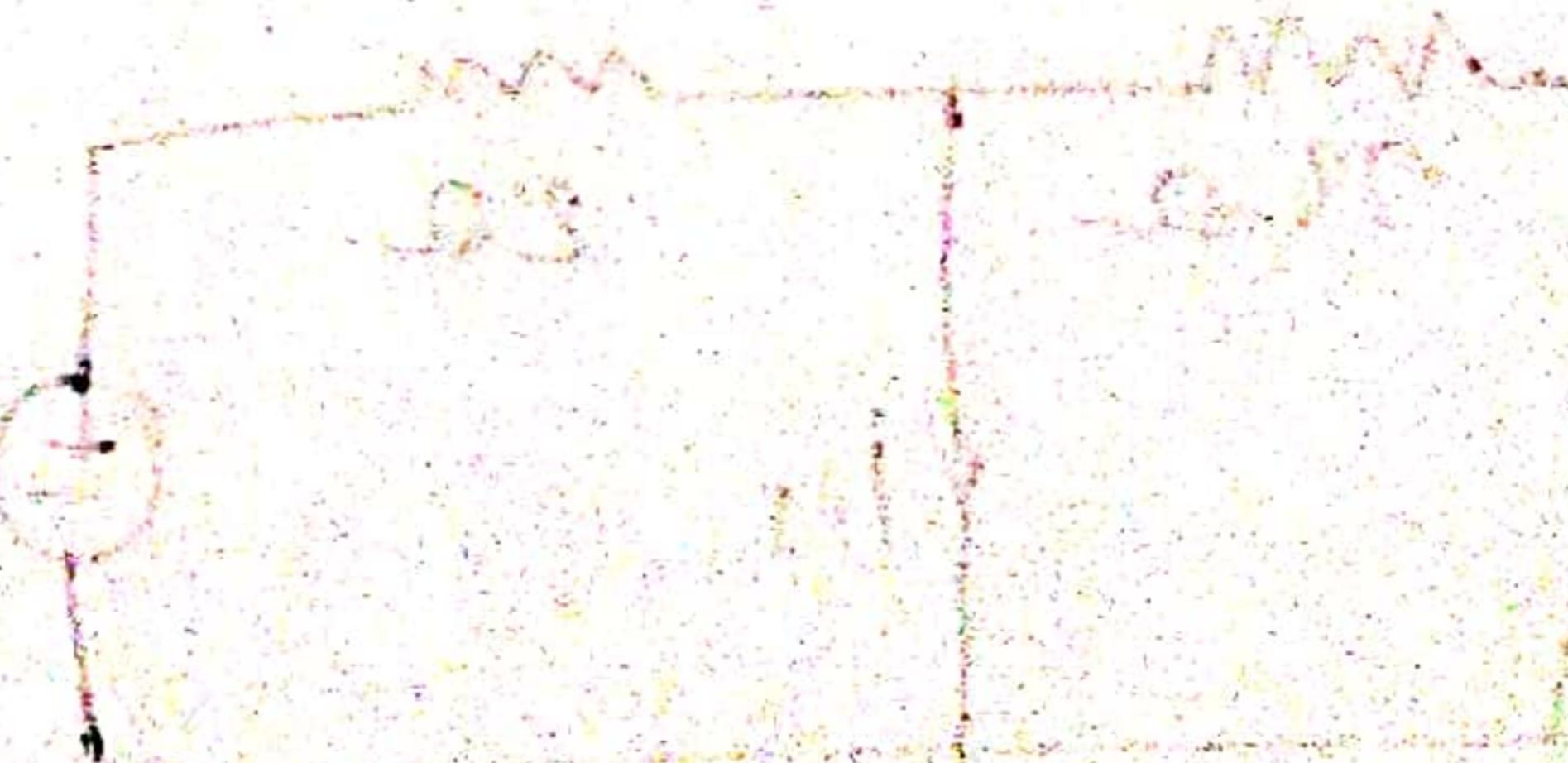


Sub:

Day

Time:

Date: / /

Ans. Q(6)

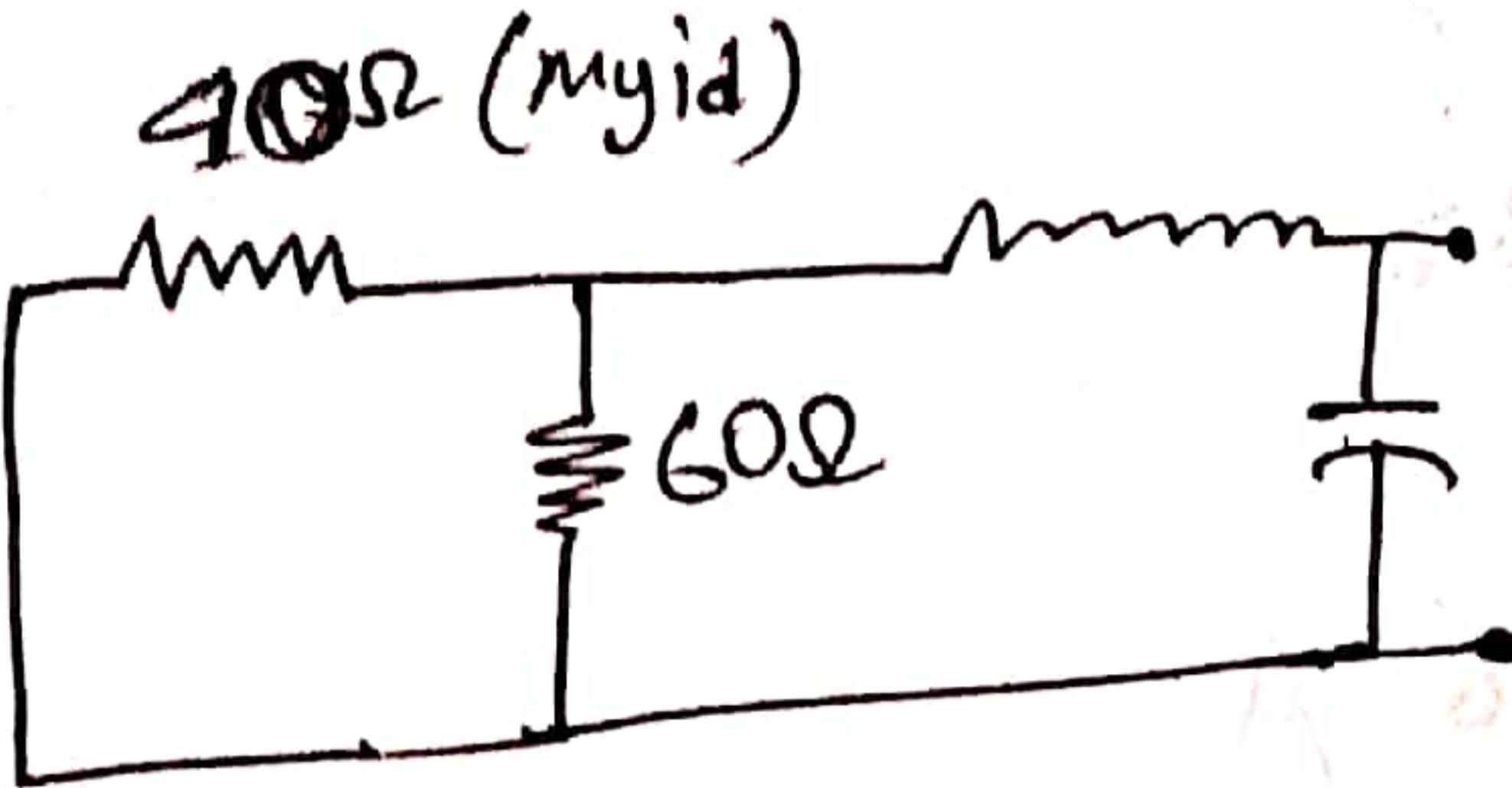

$$Z_n = Z_h = -5j \parallel [(40 + j60) + j10] \\ = -5j \parallel [13.24 + j10]$$

$$= 4.98 \angle -77.85^\circ$$

Find voltage across 60F on a mmr
 $V_{G_0\text{F}} = (120 \angle 95^\circ) \left[\frac{-60j(j10 - j5)}{90 + (60j(j10 - j5))} \right]$

$$= (120 \angle 95^\circ) \times (0.12 \angle 78.23^\circ)$$

$$V_{G_0\text{F}} = 7.2 \angle 72.5^\circ \angle 123.23^\circ$$

Now volt across diode

$$V_{aa} = (7.2 \angle 123.23^\circ) \left(\frac{-j5}{j10 - j5} \right)$$

$$= 7.2 \angle -56.77^\circ$$

Sub:

Day: _____
Time: _____ Date: _____

$$I_N = \frac{V_{12}}{Z_{12}}$$

$$= \frac{28.13 \angle -56.28^\circ}{4.88 \angle -77.65^\circ}$$

$$= 2.05 \angle 21.08^\circ A$$

Calculated value of current
in load is 2.05 A

Current is balanced

Supply voltage is 28.13 V

Supply current is 2.05 A

Supply power is 57.13 W

Supply angle is -77.65^\circ

Supply phase angle is -56.28^\circ